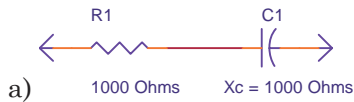


ECT150  
Homework #10 Problem Set Handout - RL, RC Phasor Analysis  
Sr. Professor Wheeler

Total Points: 24 (3 per problem)


All work must be shown, and final answers boxed or underlined. No credit if work is not shown.

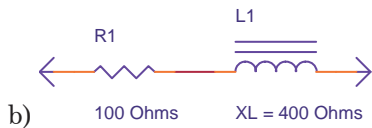1. Calculate the total impedance ( $Z_T$ ) for the following circuits. Express your answers in both rectangular and polar form. Characterize each impedance as either capacitive, inductive, or purely resistive. (State why).



$$Z_T = R - jX_C = \underline{1000 - j1000\Omega} = \sqrt{1000^2 + 1000^2} \angle \tan^{-1}\left(\frac{-1000}{1000}\right) = \underline{1.41k\Omega \angle -45^\circ}$$

Impedance is capacitive due to the negative angle caused by  $X_C$ .



$$Z_T = R + jX_L = \underline{1000 + j400\Omega} = \sqrt{1000^2 + 400^2} \angle \tan^{-1}\left(\frac{400}{1000}\right) = \underline{1077\Omega \angle 21.8^\circ}$$

Impedance is inductive due to the positive angle caused by  $X_L$ .

2. Calculate the total impedance of the circuit below at the following frequencies: 1000 Hz; 10 kHz. What happens to  $Z_T$  as frequency increases, and why?



a) At 1000 Hz:

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(1kHz)(0.02\mu F)} = 7958\Omega$$

$$Z_T = R - jX_C = \underline{10k - j7958\Omega} = \sqrt{10k^2 + 7958^2} \angle \tan^{-1}\left(\frac{-7958}{10000}\right) = \underline{12.78k\Omega \angle -38.5^\circ}$$

*(Problem 2 continued on next page)*

(Problem 2, continued):


b) At 10 kHz:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10\text{kHz})(0.02\mu\text{F})} = 795.8\Omega$$

$$Z_T = R - jX_C = \underline{\underline{10k - j795.8\Omega}} = \sqrt{10k^2 + 795.8^2} \angle \tan^{-1}\left(\frac{-795.8}{10000}\right) = \underline{\underline{10.03k\Omega \angle -4.6^\circ}}$$

c) As  $f$  increases,  $Z_T$  decreases, approaching 10 k $\Omega$  asymptotically. At 10 kHz, the capacitive reactance  $X_C$  is small compared to the series resistance. Therefore, at 10 kHz, the total impedance looks nearly resistive because the capacitor is a short to high frequencies.

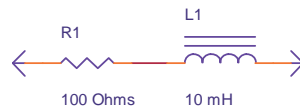3. Calculate the total impedance of the circuit below at the following frequencies: 1000 Hz; 10000 Hz. What happens to  $Z_T$  as frequency increases, and why?



a) At 1 kHz:

$$X_L = 2\pi fL = 2\pi(1\text{kHz})(10\text{mH}) = 62.83\Omega$$

$$Z_T = R + jX_L = \underline{\underline{100 + j62.83\Omega}} = \sqrt{100^2 + 62.83^2} \angle \tan^{-1}\left(\frac{62.83}{100}\right) = \underline{\underline{118\Omega \angle 32.1^\circ}}$$


b) At 10 kHz:

$$X_L = 2\pi fL = 2\pi(10\text{kHz})(10\text{mH}) = 628.3\Omega$$

$$Z_T = R + jX_L = \underline{\underline{100 + j628.3\Omega}} = \sqrt{100^2 + 628.3^2} \angle \tan^{-1}\left(\frac{628.3}{100}\right) = \underline{\underline{636.2\Omega \angle 80.96^\circ}}$$

c) As  $f$  increases,  $Z_T$  increases due to the increase in  $X_L$ . At a very high frequency,  $Z_T$  would be very high since inductors block very high frequencies. Near DC, the impedance would approach 100  $\Omega$  since that is the value of the series resistor, and inductors are shorts to DC.

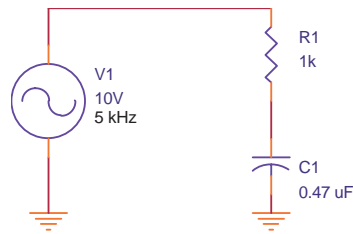4. In the circuit below, solve for  $I_T$  and  $V_{R1}$  using phasor methods. Express in both polar and rectangular form.



$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(5\text{kHz})(0.47\mu\text{F})} = 67.73\Omega$$

$$Z_T = R - jX_C = 1\text{k} - j67.73\Omega = \sqrt{1\text{k}^2 + 67.73^2} \angle \tan^{-1}\left(\frac{-67.73}{1000}\right) = 1002\Omega \angle -3.87^\circ$$

$$I_T = \frac{V_T}{Z_T} = \frac{10\text{V} \angle 0^\circ}{1002\Omega \angle -3.87^\circ} = \underline{\underline{9.98\text{mA} \angle 3.87^\circ}} = \underline{\underline{(0.00995 + j0.00067)\text{mA}}}$$

$$V_{R1} = I_T R_1 = (9.98\text{mA} \angle 3.87^\circ)(1000\Omega \angle 0^\circ) = \underline{\underline{9.98\text{V} \angle 3.87^\circ}} = \underline{\underline{(9.95 + j0.674)\text{V}}}$$


5. In the circuit of problem #4, solve for  $V_{C1}$ . Demonstrate KVL by adding  $V_{C1}$  and  $V_{R1}$  (you should get the source voltage).

$$V_{C1} = I_{C1} Z_{C1} = (9.98\text{mA} \angle 3.87^\circ)(67.73\Omega \angle -90^\circ) = \underline{\underline{0.676\text{V} \angle -86.1^\circ}} = (0.0457 - j0.674)\text{V}$$

KVL states that the sum of the rises equals the sum of the drops. By adding  $V_{C1}$  and  $V_{R1}$  we can verify this:

$$V_T = V_{C1} + V_{R1} = (0.0457 - j0.674)\text{V} + (9.95 + j0.674)\text{V} = \underline{\underline{(10 + 0j)\text{V}}} = 10\text{V} \angle 0^\circ = V_T$$

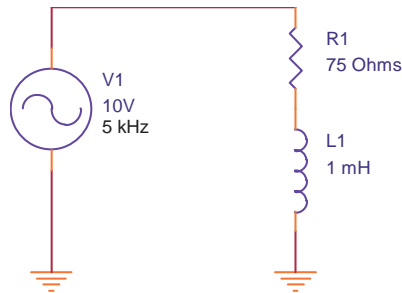6. In the circuit below, solve for  $V_{R1}$  and express in polar form.




$$X_L = 2\pi fL = 2\pi(5\text{kHz})(1\text{mH}) = 31.42\Omega$$

$$Z_T = R + jX_L = \underline{75 + j31.42\Omega} = \sqrt{75^2 + 31.42^2} \angle \tan^{-1}\left(\frac{31.42}{75}\right) = \underline{81.32\Omega \angle 22.73^\circ}$$

$$I_T = \frac{V_T}{Z_T} = \frac{10V \angle 0^\circ}{81.32\Omega \angle 22.73^\circ} = 123\text{mA} \angle -22.73^\circ$$

$$V_{R1} = I_{R1} R_1 = (123\text{mA} \angle -22.73^\circ)(75\Omega) = \underline{9.22V \angle -22.73^\circ}$$

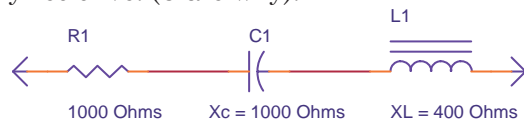
7. What is the total impedance of the circuit below? Characterize it as either capacitive, inductive, or purely resistive. (State why).



$$\text{a) } Z_T = R - jX_C + jX_L = (1000 - j1000 + j400)\Omega = \underline{(1000 - j600)\Omega}$$

b) The circuit is capacitive due to the predominance of  $X_C$  (-j600 Ohms).

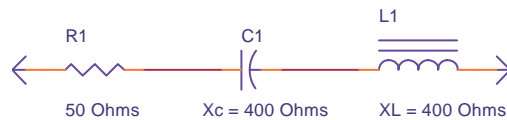8. What is the total impedance of the circuit below? Characterize it as either capacitive, inductive, or purely resistive. (State why).



$$\text{a) } Z_T = R - jX_C + jX_L = (50 - j400 + j400)\Omega = \underline{50\Omega}$$

b) The circuit is purely resistive. There is no  $X_C$  or  $X_L$ .