


ECT150
Homework #5 Solution Set
Sr. Professor Wheeler

Handout Problems on Parallel Circuits

Total Points: 27 (3 per problem)

All work must be shown, and final answers boxed or underlined. No credit if work is not shown.

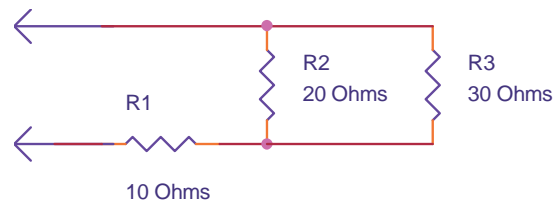
1. What is the total resistance of the circuit below?



The total resistance can be found by:

$$R_T = 20\Omega \parallel 30\Omega + 10\Omega = \frac{20\Omega \times 30\Omega}{(20\Omega + 30\Omega)} + 10\Omega = \underline{\underline{22\Omega}}$$

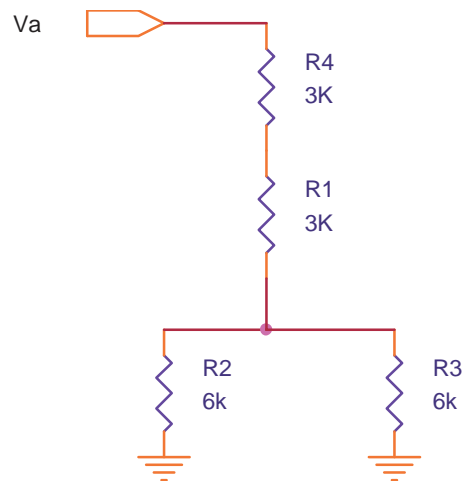2. What is the total resistance of the network below as measured between point Va and ground?




$$R_T = R4 + R1 + (R2 \parallel R3) = 3k + 3k + (6k \parallel 6k) = \underline{\underline{9k\Omega}}$$

3. Calculate the following for the figure below:

a) I_T

b) R_T

c) V_A

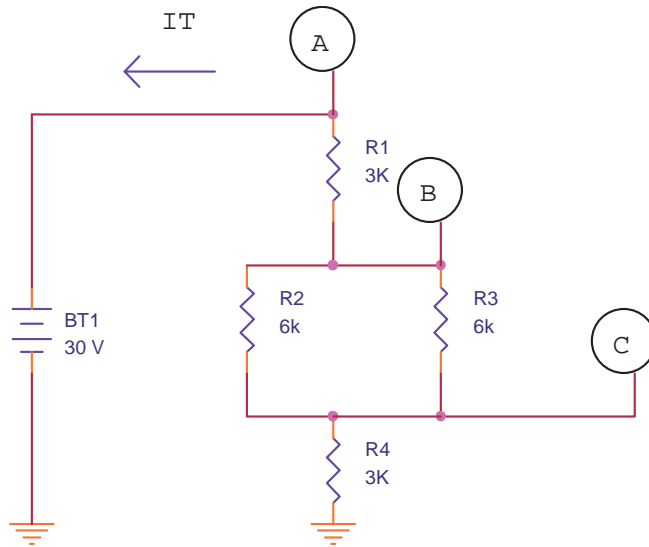

$$a) I_T = \frac{V_T}{R_T} = \frac{30V}{R1 + R4 + (R2 \parallel R3)} = \frac{30V}{9k\Omega} = \underline{\underline{3.33mA}}$$

$$b) R_T = R1 + R4 + (R2 \parallel R3) = 3k + 3k + (6k \parallel 6k) = \underline{\underline{9k\Omega}}$$

c) By inspection, $V_A = V_{BT1} = \underline{\underline{30V}}$ since it is connected directly to the battery positive.


4. Use the current divider rule to find the current I_{R2} in the figure above. Calculate the voltages at points B and C using any available method.

$$a) I_{R2} = I_T \left(\frac{R3}{R2 + R3} \right) = (3.33mA) \left(\frac{6k}{6k + 6k} \right) = \underline{\underline{1.67mA}} \text{ (Half, since } R2 = R3 \text{)}$$

$$b) V_B = V_T \left(\frac{(R2 \parallel R3) + R4}{(R2 \parallel R3) + R1 + R4} \right) = 30V \left(\frac{6k}{9k} \right) = \underline{\underline{20V}} \text{ (By the voltage divider rule)}$$


$$c) V_C = V_{R4} = I_{R4} R4 = (3.33mA)(3k) = \underline{\underline{10V}} \text{ (By Ohm's law, } I_{R4} = I_T \text{)}$$

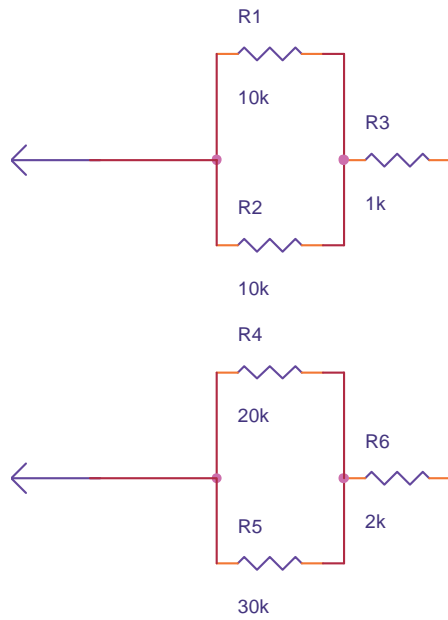5. Find the total resistance of the circuit below.



$$R_T = (R1 \parallel R2) + R3 + R6 + (R4 \parallel R5) = 10k \parallel 10k + 1k + 2k + 20k \parallel 30k = \underline{\underline{20k\Omega}}$$

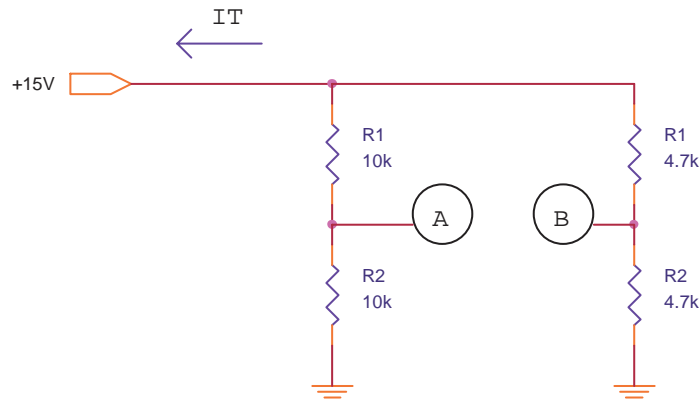
6. The circuit below is a Wheatstone bridge. What will the current I_T be when the circuit is connected to a +15V source?



(Note: The four resistors above should be labeled R1, R2, R3, R4!)

$$I_T = I_1 + I_2 = \frac{15V}{(10k + 10k)} + \frac{15V}{(4.7k + 4.7k)} = \underline{\underline{2.35mA}}$$

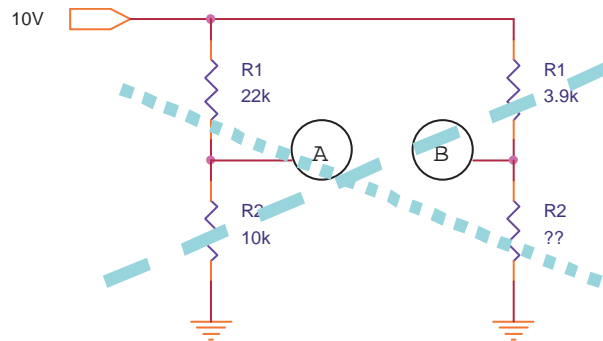7. A Wheatstone bridge is balanced when the voltage V_{AB} is zero. What value of R2 will balance the Wheatstone bridge below? (Use the bridge balance equation, OR Ohm's law to solve for the value of R2 that will make V_B the same as V_A).




(Again, the four resistors should be labeled R1-R4). For any bridge, the product of the “cross arms” is set equal:

$$R_2 R_1' = R_1 R_2'$$


$$R_2' = \frac{R_2 R_1'}{R_1} = \frac{(10k)(3.9k)}{22k} = \underline{\underline{1.77k\Omega}} \quad (\text{Where } R_1' \text{ and } R_2' \text{ refer to the right-hand resistors})$$

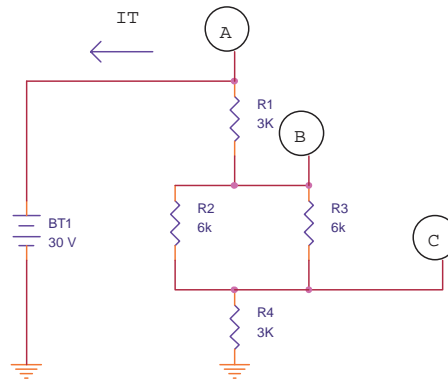8. Calculate the power of each resistor in the figure for problem #3, and the total power. (There will be five resulting answers).



- a) $P_{R1} = I_T^2 R1 = (3.33mA)^2 (3k) = \underline{33.3mW}$
- b) $P_{R2} = I_{R2}^2 R2 = \left((3.33mA) \frac{R3}{R2 + R3} \right)^2 (6k) = \underline{16.67mW}$ (Using the current divider rule)
- c) $P_{R3} = P_{R2} = \underline{16.67mW}$ By inspection since $R2=R3$ and $I_{R2} = I_{R3}$
- d) $P_{R4} = I_T^2 R4 = (3.33mA)^2 (3k) = \underline{33.3mW}$ (Could also be same as P_{R1} by inspection)
- e) $P_T = V_T I_T = (30V)(3.33mA) = \underline{100mW}$ (Could also add up $P_{R1} - P_{R4}$)

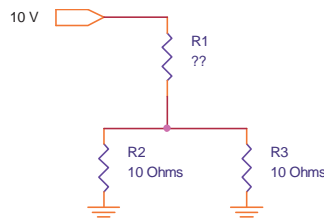9. In the figure below, calculate the value of R_1 that will cause the total circuit power to be 10 watts.



Explanation of method: Find the current that would be drawn from the 10V source to dissipate 10 watts, then calculate the total resistance that gives that current; then work backwards from the total resistance to get R_1 .

$$I = \frac{P}{V} = \frac{10W}{10V} = 1A$$

$$R_T = \frac{V}{I} = \frac{10V}{1A} = 10\Omega$$

$$R_T = 10\Omega = R2 \parallel R3 + R1$$

$$\therefore R1 = 10\Omega - R2 \parallel R3 = 10\Omega - 5\Omega = \underline{5\Omega}$$