

ECT150
Homework #2 Key
Sr. Professor Wheeler

Chapter 3 problems 1-24

Total Points: 24

All work must be shown, and final answers boxed or underlined. No credit if work is not shown.

1. If voltage is doubled (2x) and resistance is halved (1/2x), the new current will be 4 times the original value.
2. If the current triples but the resistance stays the same, what happens to the power?


$P_1 = I^2 R$ describes the original power, and

$P_2 = (3I)^2 R$ describes the power with the current tripled; therefore:

$$\frac{P_2}{P_1} = \frac{(3I)^2 R}{I^2 R} = \frac{9I^2 R}{I^2 R} = 9$$


The power increases by a factor of 9.

3. The circuit looks like this:

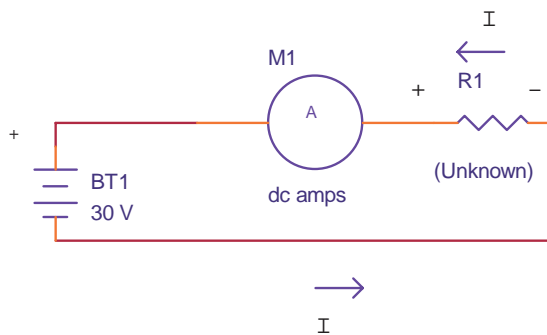

The resistance is found by:

$$R = \frac{V}{I} = \frac{30V}{2mA} = \underline{\underline{15k\Omega}}$$

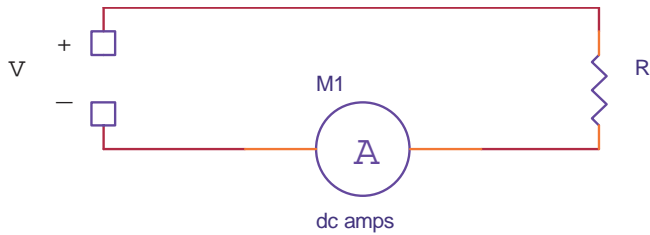

(Figure 3-17, used for questions 4-21)

4. Given: $V=50V$, $R=33K$; Find: I

$$I = \frac{V}{R} = \frac{50V}{33K} = \underline{\underline{1.52mA}}$$

5. Given: $I=3\text{ mA}$, $R=12K$; Find V

$$V = IR = (3mA)(12K) = \underline{\underline{36V}}$$

6. How will the items change if the voltage in question 5 were doubled?

- a) V will double (“Who is buried in Grant’s tomb?”)
- b) R will remain the same
- c) I will double since current is directly proportional to voltage

7. Given $I=50\text{ mA}$ and $V=41\text{ V}$; Find R

$$R = \frac{V}{I} = \frac{41V}{50mA} = \underline{\underline{820\Omega}}$$

8. Given: $P=100\text{ mW}$, $I=12.5\text{ mA}$; Find V

$$P = V \times I$$

$$\therefore V = \frac{P}{I} = \frac{100mW}{12.5mA} = \underline{\underline{8V}}$$

9. Given: $R=10\ \Omega$, $P=100W$; Find: I

$$P = I^2 R$$

$$\therefore I = \sqrt{\frac{P}{R}} = \sqrt{\frac{100W}{10\Omega}} = \underline{\underline{3.16A}}$$

10. Given: $P_{\text{original}}=180\text{ W}$, and the current falls to $1/3$ its original value; Find P_{new}

$$P_1 = I_1^2 R = 180\text{W}$$

$$P_2 = I_2^2 R = ???$$

$$\frac{P_1}{P_2} = \frac{I_1^2 R}{I_2^2 R} = \left(\frac{I_1}{I_2}\right)^2$$

$$I_2 = \frac{I_1}{3}$$

$$\therefore P_2 = P_1 \left(\frac{I_2}{I_1}\right)^2 = 180\text{W} \left(\frac{(I_1/3)}{I_1}\right)^2 = 180\text{W} \left(\frac{1}{3}\right)^2 = \underline{\underline{20\text{W}}}$$

Note to students: This looks complicated, but it is really just demonstrating that power is proportional to the *square* of current.

11. Given: $V=100\text{ V}$; Find the value of R that will “limit” the current to 8.5 mA

$$R = \frac{V}{I} = \frac{100\text{V}}{8.5\text{mA}} = \underline{\underline{11.764\text{K}\Omega}}$$

12. Given: Original voltage = 100 V , original resistance = 25k .
Find: The current if V is doubled and R is tripled.

$$V_{\text{new}} = V \times 2 = 200\text{V}$$

$$R_{\text{new}} = R \times 3 = 75\text{k}$$

$$I_{\text{new}} = \frac{V_{\text{new}}}{R_{\text{new}}} = \frac{200\text{V}}{75\text{k}} = \underline{\underline{2.67\text{mA}}}$$

13. The power will increase if V and R are both doubled; the reason is that power is $\frac{V^2}{R}$; if both V and R are doubled, the power becomes $(4/2)$ or *twice* its original value.

14. Given: $V=150\text{ V}$, $R=8\text{k}$; Find: I

$$I = \frac{V}{R} = \frac{150\text{V}}{8\text{K}} = \underline{\underline{18.75\text{mA}}}$$

15. Find the power dissipated by the circuit of problem 14.

$$P = \frac{V^2}{R} = \frac{150\text{V}^2}{8\text{K}\Omega} = \underline{\underline{2.81\text{W}}}$$

16. Given the data of problem 14, express the energy (in Watt-Hours) that the circuit will consume over a period of 3 hours.

$$\text{Energy} = \text{Power} \times \text{Time} = (2.81\text{W}) \times (3 \text{ Hr}) = \underline{\underline{8.43 \text{ W-H}}}$$

17. Given: $V=250 \text{ V}$, $R=12 \text{ k}$; Find: I

$$I = \frac{V}{R} = \frac{250\text{V}}{12\text{K}} = \underline{\underline{20.83\text{mA}}}$$

18. Find the power under the conditions of problem 17.

$$P = \frac{V^2}{R} = \frac{250\text{V}^2}{12\text{K}\Omega} = \underline{\underline{5.21\text{W}}}$$

19. Given the data of problem 17, express the energy (in Watt-Hours) that the circuit will consume over a period of 6.5 hours.

$$\text{Energy} = \text{Power} \times \text{Time} = (5.21\text{W}) \times (6.5 \text{ Hr}) = \underline{\underline{33.87 \text{ W-H}}}$$


20. Given: $V=100 \text{ V}$, $P=50 \text{ mW}$; Find: R

$$P = \frac{V^2}{R}$$
$$\therefore R = \frac{V^2}{P} = \frac{100\text{V}^2}{50\text{mW}} = \underline{\underline{200\text{K}\Omega}}$$

21. Given: $P=100 \text{ mW}$, $R=10\text{k}$. Find; V

$$V = \sqrt{PR} = \sqrt{(100\text{mW})(10\text{k}\Omega)} = \underline{\underline{31.6\text{V}}}$$

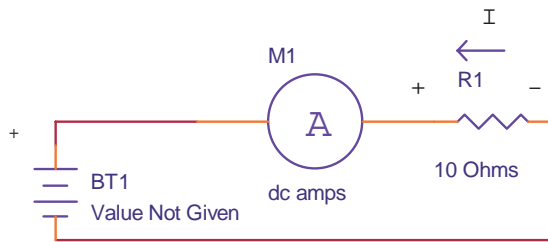22. Draw a schematic diagram showing a source, a resistor, and an ammeter. Assume the power dissipation is 1000W and the resistance is 10 Ohms. Solve for the current I.



$$P = I^2 R$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{1000W}{10\Omega}} = \underline{\underline{10A}}$$

23. Calculate the applied voltage for problem 22.

$$V = IR = (10A)(10\Omega) = \underline{\underline{100V}}$$

24. Label all the parameters on the circuit diagram for question 22 and indicate the direction of current flow throughout the circuit, and the polarity of voltages across each component.

