

A Microcontroller-Based Precision Xenon Strobe System

Tom Wheeler, N0GSG
twheeler@kc.devry.edu
January 2005

WARNING

The circuitry described in this paper produces voltages of more than 350 volts and utilizes potentially lethal energy levels. Do not construct this project without appropriate knowledge and safety procedures. If you don't have the background to do this project safely, get qualified assistance!

Introduction

There are many applications where a precisely-controlled high-intensity xenon strobe system comes in very handy. In photography, a precision strobe will let you accurately capture motion and velocity, and realize effective remote control for "slave" strobe systems (using an IR or RF data link). Strobes can be setup for measuring the timing of events in machinery, and even used as wireless signaling devices (such as in traffic preemption systems).

The circuit described in this paper is a microprocessor-controlled precision strobe that operates from a 10 to 16 V DC supply (requiring less than 2A for typical operation). It uses an Atmel AT90S2313 single-chip microcontroller to develop the timing signal. The '2313 was chosen because it has an onboard UART, which would be very useful for adapting this project to a remote or PC-controlled setup. Only two I/O pins of the microcontroller are used! Timing is derived from a 4.9152 MHz crystal.

Circuit Analysis

Figure 1 shows the entire circuit. There are three primary sections, a DC to DC step-up inverter, the microcontroller, and a trigger circuit for the xenon flash tube.

The inverter circuit is composed of four transistors, Q_1 through Q_4 . Q_2 and Q_3 form a push-pull multivibrator with a frequency of about 880 Hz. The outputs at the collectors of Q_2 and Q_3 are approximately square waves with a 180 degree phase difference. The square wave outputs directly drive the gates of power MOSFETs Q_1 and Q_4 , resulting in an AC square wave signal driving the primary of T_1 , the step-up transformer, which is a standard 12V CT @3A to 120 V unit. The output of T_1 is fed into the voltage doubler, which consists of C_7 , C_9 , D_2 , and D_1 , resulting in a resting voltage of about +390 V across C_9 . The prototyped inverter was better than 95% efficient -- *no* heatsinks are needed on Q_1 and Q_4 in this application!

The value of C_9 controls the amount of energy delivered to the flash tube for each flash, which can be calculated by:

$$(1) PE = \frac{1}{2} C_9 V_Q^2$$

Where C_9 is the value of the "dump" capacitor, and V_Q is the standing (quiescent) voltage at firing time (about 390 V in this circuit). For safety, you should evaluate the amount of energy being driven into the flashtube you intend to use and make sure that the ratings aren't being exceeded at the flash rate.

The microcontroller is comprised of U_2 , the AT90S2313. The MCU is provided regulated 5 volts by U_1 , and Y_1 determines its operating frequency. The value of 4.9152 MHz provides optimum choice of data rates for the UART, should a serial interface be implemented for the unit. Port output PB0 provides the trigger signal for the strobe; this signal is current boosted by Q_5 prior to driving the trigger stage. Pin PD0 is used as an external input; the system soft-switches between internal and external trigger by examining this pin during initialization.

On power-up the software examines the state of pin PD0, which is connected to the EXT IN connector through an ESD suppression network (R_{11} , C_{15}) and a pull-up resistor (R_{10}). If this signal measures "1," then the processor simply accepts an input signal from J_1 and passes it out through PB0 to trigger the strobe. If the MCU sees a "0" on PD0 during power-up, it begins firing the flash at a rate determined by the software timing loop (up to 30 seconds total).

The trigger circuit consists of Q_6 , C_{11} , R_7 , and T_2 . Initially, Q_6 is non-conductive (off) and C_{11} charges to at least 300 V through R_7 . When a trigger current is applied to the gate of Q_6 , it turns on, rapidly dumping the charge from C_{11} into the primary of T_2 , which then steps the pulse up to approximately 4 kV. The 4 kV pulse is applied to the trigger electrode of the xenon flash tube; the pulse provides enough ionization of the xenon gas to allow the tube to fully conduct, pulling the energy from C_9 . Q_6 turns off as C_{11} discharges ($I_{\text{HOLD-}Q_6} < (V_{\text{HV}} / R_7)$), and the tube ceases conducting once the anode to cathode voltage falls below about 40 volts, preparing the circuit for another firing cycle. Resistor R_6 helps guarantee lamp commutation (shut-off), but may be omitted to obtain higher speed strobes (the circuit can easily operate over 40 Hz even with R_6 in place). The typical pulse width of the emitted light beam is much less than 500 μs .

Construction

The circuit was built on two printed circuit boards layed out using EAGLE CAD, but could easily be constructed using conventional point-to-point methods. The inverter and microprocessor were placed on one board, and the xenon lamp and high-voltage trigger circuitry were placed on the second board. This was done to allow the circuitry to fit into a desired enclosure (a discarded hand-held spotlight case, which provides a useful reflector and insulation from the high voltage circuitry).

Don't skimp on the high voltage capacitors; this circuit provides sufficient output power (better than 40W, easily) to destroy underrated components in a flash! C_9 should be temperate rated at 100 °C. **Make absolutely certain that the high voltage components are untouchable by the user.** Note that the ground of the circuit is common between the low and high-voltage sections; there's no particular need for isolation here.

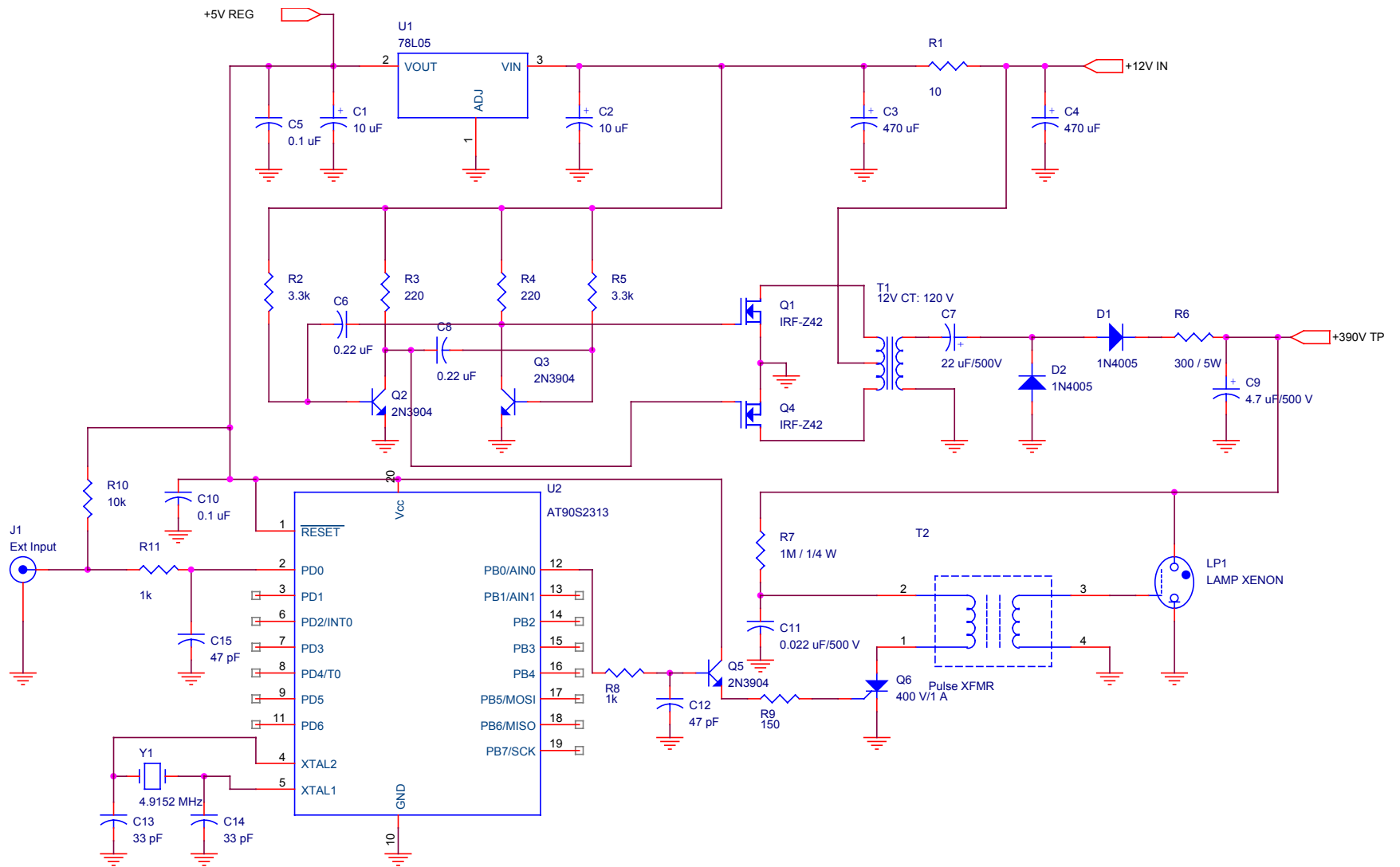


Figure 1: Schematic diagram of the precision strobe system

Software

You'll need software to drive the microcontroller. The prototype software simply flashes the strobe at a predetermined rate for around 25 seconds, then shuts off the preserve the flash tube and high voltage components. By adjusting the constants in the listing, you can obtain very precise flash rates. You will probably want to modify the code for your particular purpose. Because the circuit is based on a crystal oscillator, the frequency will be very precise.

Of course, if you already have a precise frequency source, you can dispense with the microcontroller and directly fire the strobe by triggering the base of Q_5 .

Listing 1 shows the code as implemented in the prototype unit. Note that some functions may not be directly called. This is because the software is built around a standardized application framework for this particular processor which has the commonly-needed functions built in.

Conclusion

A precision strobe system need not be expensive. The unit detailed in this article is reliable, efficient, and flexible in its operation. It should be useful in many fields of study.

```

; LISTING 1: strobe.asm
;
; Controller for precision strobe.
;
; Target: AT90S2313 (ATMEL), 4.9152 MHz clock
;
; Version 1.0
;
; Author: Wheeler, T (NOGSG)
;
;
; I/O Pin Descriptions:
;
; PB0: OUTPUT, Strobe pulse to fire xenon tube; fires on L-H transition.
; PB1-PB7: OUTPUTS, Unused
;
; PD0: INPUT. Checked on power up. If (PD0==0), then strobe mode is entered. If
;         (PD0==1), external input mode is entered.
;
; Note: The internal trigger frequency is 19.2582 (+/- 0.001 Hz) in this version.
;
; PD1-PD6: OUTPUT, UNUSED
;
; Register Usage:
;
; R10: Last Switch Status. Holds result from last state change of switch on PD3;
;      used to determine which way to program INT1 edge-sensitivity.
;

.equ   portd=$12
.equ   ddrd=$11
.equ   pind=$10
.equ   portb=$18
.equ   ddrb=$17
.equ   eecr=$1c
.equ   eedr=$1d
.equ   eear=$1e
.equ   pinb=$16
.equ   acsr=$08
.equ   tccr0=$33
.equ   tcnt0=$32
.equ   mcucr=$35
.equ   gimsk=$3b
.equ   timsk=$39
.equ   sreg=$3f
.equ   udr=$0c
.equ   ucr=$0a
.equ   ubrr=$09
.equ   usr=$0b
.equ   tcclra=$2f
.equ   tcclrb=$2e
.equ   tcntlh=$2d
.equ   tcntl1=$2c
.equ   ocrlah=$2b
.equ   ocrlal=$2a
.equ   icrlh=$25
.equ   icrl1=$24

.equ   spl=$3d
.equ   RAMHIGH=$df
.equ   RAMLOW=$60

.equ   TEMPBUF=$c0
.equ   FRAMEBUF=RAMLOW           ;frame buffer
.equ   INPUTBUF=RAMLOW+80       ;line-input buffer
.equ   MAXDATA=64                ;maximum number of data bytes allowed in a frame

```

```

.org 0 ;code always begins at address 0
rjmp start
rjmp ext_int0
rjmp ext_int1
rjmp timer1_capt1
rjmp timer1_compl
rjmp timer1_ovf1
rjmp timer0_ovf
rjmp uart_rx
rjmp uart_dre
rjmp uart_tx
rjmp ana_comp

;
; dummy stubs for interrupt service routines
;

ext_int0:      reti

;
; External Interrupt 1 handler.
;

ext_int1:      reti

timer1_capt1:
timer1_compl:
timer1_ovf1:
timer0_ovf:
uart_rx:
uart_dre:
uart_tx:
ana_comp:      reti

;
; MAIN BODY OF PROGRAM
;

;***** main *****
;
;
;
;*****
;
;

start: ldi    r16, RAMHIGH
      out    spl, r16 ;initialize stack to top of RAM

      rcall  initports_run ;port b/d setup for RUN mode

      rcall  init_timer
      rcall  init_timer1 ;initialize timers

;
; check PD0 status for external input
;

st1:  ldi    r16, 1 ;1/2 second wait
      rcall  waitR16seconds
      in    r16, pind ;test EXT IN
      bst   r16, 0
      brts  ext_input ;if (PD0==1) use external input

```

```

;
; 19.2582 Hz strobe routine with 30-second timeout
;

main_prog:

    ldi    r16,1        ;initial value of PB0 output
    ldi    r17,1        ;value for toggling PB0 output

;
; *** Flash time limiter. Runs for up to 420 flashes (about 30 seconds)
; before auto-shut off.
;

    ldi    r20,4
    ldi    r21,112      ;Max 30 seconds (420 flashes)

main_loop:
    eor    r16,r17      ;toggle PB0
    out    portb,r16    ;write the result

;
; Delay loops. f=14.025 Hz, T=0.071301247772 s,
; T/2 = 35,650.6238 us
;

    ldi    r19,166      ;do 165 loops
                                ;2+165(767+3) T
                                ;total for outer, inner loops

wait_outer:
    ldi    r18,$ff      ;inner loop = 255*3 + 2 T
wait:   dec    r18
        brne   wait

        dec    r19
        brne   wait_outer

;
; This code uses up the remaining 560T
;

    ldi    r18,40       ;187*3 + 2 T = 560 T
wait2:  dec    r18
        brne   wait2

;
; *** Timer for auto-shutoff here. ***
;
; Counts down from the assigned limit value, then shuts off the strobe when this is
; reached.
;

    dec    r21
    brne   main_loop
    dec    r20
    brne   main_loop

```

```

;
; 30 seconds have passed, shut it off
;
;

        clr    r16
        out    portb,r16

end:    rjmp   end            ;that's all

;
; Ext input routine. NO time limit!
;

ext_input:
        in     r16,pind
        andi   r16,$01        ;isolate PD0
        out    portb,r16
        rjmp   ext_input

;
; Wait for the number of half-seconds specified by R16.
;
;
WaitR16Seconds:
        ldi    r17,$60

WaitR16Seconds_Inner:
        ser    r24            ;about 3 mS delay
        rcall  wait_r24
        dec    r17
        brne   WaitR16Seconds_Inner

        dec    r16
        brne   WaitR16Seconds

        ret

;
;Wait for the number of Timer/Counter0 cycles specified by R24.
;R25 is altered.
;Timer/Counter0 must be initialized before calling.
;

wait_r24:
        clr    r25
        out    tcnt0,r25
wr24:   in     r25,tcnt0
        cp     r25,r24
        brlo   wr24
        ret

```